

ADLD COURSE PROJECT

TEAM-21


Team members:

- * Aditi V Angadi – 01FE19BEC212
- * Venkatesh Kulkarni – 01FE19BEC131
- * Prathamesh Rane – 01FE19BEC294

 1) Problem Statement :


License Plate Recognition System.

A license plate is a series of letters, numbers, or a combination of both that is a registration of a vehicle's identity. Usually, a license plate is on a rectangular metal plate and is required to be both on the front and back of the vehicle.



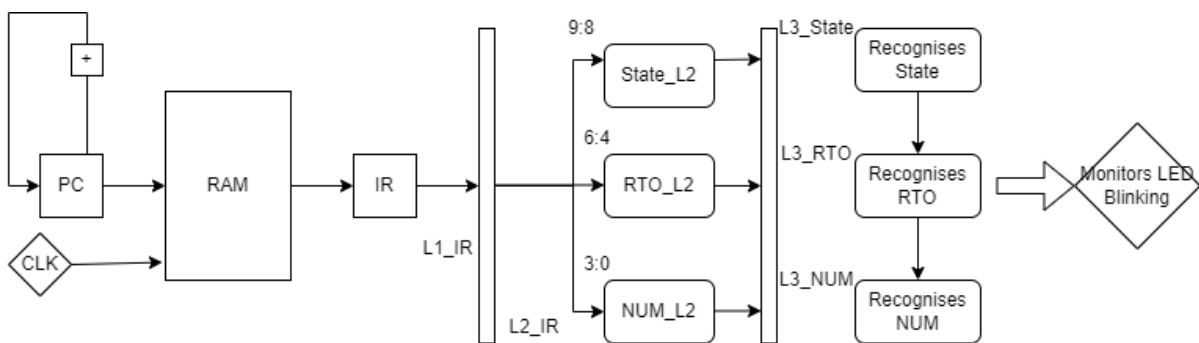2) Architecture :

We have used 3 stage pipeline architecture. This is an architecture implementation technique that allows multiple instructions to overlap in execution. The processor is organized as a number of stages that allow multiple instructions to be in various stages of their instruction cycle.



3) Algorithm :

- Here we are taking Number plate to be of 9 bits i.e., 4 MSBs represent plate number(0-3) , next 3 bits represent RTO number(4-6) , next 2 bits represent State(7-8). Total vehicles = 512.
- State : KA, GJ, BR, MH
- RTO number : rto1, rto2, rto3, rto4, rto5, rto6, rto7, rto8.
- Plate number : person1, person2, person3, person4, person5, person6, person7, person8, person9, person10, person11, person12, person13, person14, person15, person16.
- Memory has 4 number plate info stored.


- a) Initially in memory program counter(pc=0).
- b) Step 1 : In pipeline stage 1, L1_IR instruction fetches the mem[pc] then it increments pc.
- c) Step 2 : In pipeline stage 2, number plate info is decoded to L2_State, L2_RTO, L2_NUM from L2_IR.
- d) Step 3 : In pipeline stage 3, execution takes place through L3_State, L3_RTO, L3_NUM.
- e) Then L3_State is checked by case statement if it's KA then it checks the RTO. Then it checks with plate number.
- f) Same checking happens with other states and other RTOs.
- g) Output is Monitored by LEDs. Combination of LEDs is blinked based on the output (License Plate Recognition) generated.

4) Simulation :

Waveform of the system is seen as shown below when obtained from Xilinx ISim Simulator .


Here we can also see that after 3 clock cycles output execution starts which indicates that we are going through 3- stage pipelined architecture.

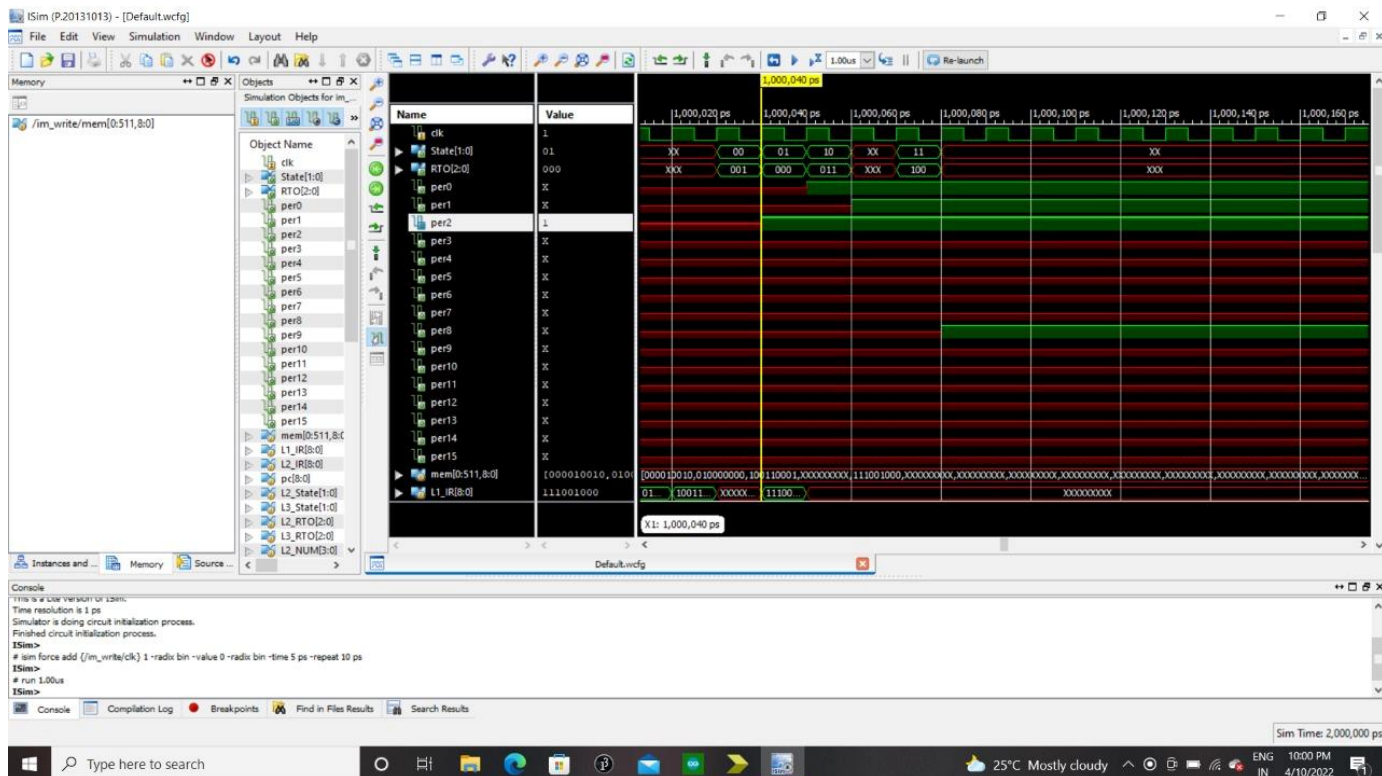
For the first `mem[0] = 9'b000010010` , we can see that outputs indicates that this vehicle is from {KA RTO2 person3} i.e., State = {00} indicating State KA and RTO = {001} indicating RTO2 .



 5) Synthesis :

Below is the RTL Schematic obtained when we synthesize the Verilog code in Xilinx Software



 

6) HDL Synthesis Report :-

Macro Statistics

# Registers	: 24
1-bit register	: 16
2-bit register	: 2
3-bit register	: 2
4-bit register	: 2
9-bit register	: 2
# Multiplexers	: 16
1-bit 4-to-1 multiplexer	: 16